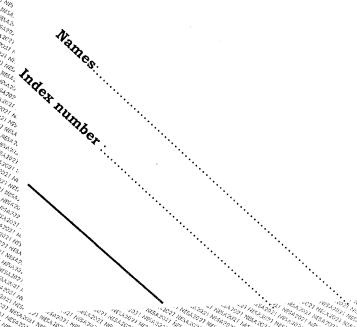


AES – Vehicle drive assistance and

Electronic system

T161

Friday, 23/7/2021 08:30 - 11:30 AM



TVET NATIONAL EXAMINATION, RTQF LEVEL 5, 2020-2021

QUESTIONS and ANSWERS BOOKLET

AUTOMOBILE ELECTRICITY AND OPTION/TRADE:

ELECTRONICS SYSTEMS


 $\underline{\mathrm{SUBJECT}}$: Vehicle drive assistance and Electronic system

ACADEMIC YEAR: 2020-2021

Read carefully the instructions on page (i) & (ii).

FOR EXAMINER'S USE ONLY

			I OIC Z				Т	1	T	T	
QUESTIONS	1	2	3	4	5	6	7	8	9	10	Total
QOESTIONS	-		-								
Marks			SA 75 PS 90						10	20	Total
QUESTIONS	11	12	13	14	15	16	17	18	19	120	Total
Marks											
					OF.	26	27	28	29	30	Total
QUESTIONS	21	22	23	24	25	120			-		
Marks											
				*00, Me, 30	2/46/202/4	6 1 205 No. 1	3027 4KE 302	1 485 4027 MG	142021 ARS 420	22) M2 42021	16 420 27 W. 420 34 7027 W. 420

 

TVET NATIONAL EXAMINATION, RTQF LEVEL 5, 2020-2021

INSTRUCTIONS TO CANDIDATES: PART I (Answer Booklet)

- 1. A candidate should fill in the actual names and the index number on the cover of this questions and answer booklet on the provided place (Black Box).
- 2. It is illegal for a candidate to write any of his/her names, index number or a school name inside the answer booklet.
- 3. A candidate should check if all pages of the answer booklet are complete. No candidate should remove or tear any pages or part of it from the answer booklet.
- 4. A candidate should answer in the language in which the examination is set. (See page (ii))
- 5. A candidate should sign on the sitting plan when submitting the answer booklet. He/she has also to check if the answer booklet is well sealed.
- 6. No extra paper is allowed in the examinations room. If a candidate is caught with it his/her results will be nullified.
- 7. No candidate is allowed to write answers not related to the subject being sat for, otherwise it will be considered as a cheating case.
- 8. Write your answers on the 12 lined pages (From page 1 of 12 to page 12 of 12).
- 9. Use the last non-lined pages as draft.
- 10. Results for any candidate who is caught in examination malpractices are nullified. The cheating can be recognized during examinations administration, marking exercise or even thereafter.

TVET NATIONAL EXAMINATION, RTQF LEVEL 5, 2020-2021

OPTION/TRADE: AUTOMOBILE ELECTRICITY AND ELECTRONICS SYSTEMS

SUBJECT: Vehicle drive assistance and Electronic system

DURATION: 3 hours

INSTRUCTIONS TO CANDIDATES: PART II (Question Paper)

The paper is composed of two (2) Sections as follows:

Section I: Attempt all the Twelve (12) questions

(60 marks)

Section II: Attempt any Four (4) questions out of Six (6)

(40 marks)

Allowed materials:

- Ruler or square
- Calculator

Note:

Every candidate is required to carefully comply with the provided assessment instructions.

(ii)

State any five (5) advantages of advanced driver assistance
 marks

2. Identify five (5) components of vehicle cruise control system.

5 marks

3. What are the components of parking assistance system?

5 marks

4. Mention any five (5) operating features for adaptive cruise5 marks

5. What are components does airbag system contain?

5 marks

6. Differentiate analogue instrument from digital instrument.

5 marks

7. List five (5) different electrical and Electronics accessoriessystem of motor vehicle.5 marks

- 8. State any five (5) components of immobilizer system components.5 marks
- **9.** The voltage measured across three 3 resistors connected in series are **5V**, **7V**, and **10V**; 2A supply current. Determine:
 - a) The supply voltage
 - b) The total circuit resistance.

5 marks

- 10. The resistor of 20 ohms, 20 ohms and 30ohms are connected in parallel. What is the resistance must be added within combination to obtain a total resistance of 10 ohms, if the complete circuit expends a power of 0.36 KW at the total current flowing?
 5 marks
- 11. Identify five (5) components of power mirror 5 marks
- 12. State all things which can trigger car alarm in motor vehicle.

5 marks

Section II: Attempt any Four (4) questions out of Six (6)


(40 marks)

13. Explain ten (10) types of computers used in the cars.

10 marks

- 14. a) Draw a simple motor reverse circuit.
 - b) i) What is the name of the figure below?
 - ii) Name the parts of the figure below.

10 marks

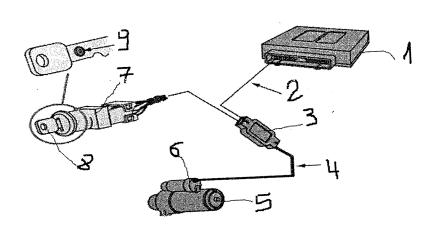

15. Draw the circuit diagram of exterior mirrors control system.

10 marks

- **16. a)** Name five (5) components of vehicle adaptive cruise control system.
 - b) State at least ten (10) problems of cruise control systemand their possible causes.10 marks

- 17. a) What is the role of vehicle parking assisted system?
 - **b)** State any four (4) functions of vehicle parking assisted system.
 - c) Name five (5) components of vehicle parking assisted system.
 10 marks
- 18. Identify the assemblage of an alarm system. 10 marks

				/ Account of the second of the
A TO A MERCANIA MENTANTAN	MEGAZI MEGAZI MEGAZI MEGAZI MEGAZI MEGAZI MEGAZI MEGAZI			
	4313)			
		TO STATE OF		